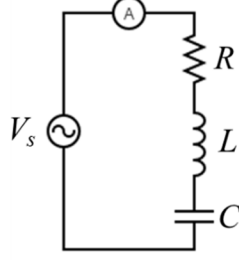


## Q factor and bandwidth of RLC resonant circuit

The Q-factor of a system is defined as  $Q = \frac{2\pi \times \text{stored energy}}{\text{dissipated energy per cycle}}$  (at resonance).

We now have the RLC resonant circuit as



The current amplitude is

$$I = \frac{V_s}{Z_{tot}} = \frac{V_s}{R + j\left(\omega L - \frac{1}{\omega C}\right)} \Rightarrow |I| = \frac{|V_s|}{\sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}} = \frac{|V_s|/R}{\sqrt{1 + \left(\omega L - \frac{1}{\omega C}\right)^2/R^2}}.$$

Let the current be  $I(t) = |I|e^{i\omega t}$ , i.e., its phase is 0.

The voltage on the capacitor is then  $V_c(t) = IX_c = \frac{|I|}{j\omega C} e^{i\omega t} = \frac{|I|}{\omega C} e^{i\left(\omega t - \frac{\pi}{2}\right)}$ .

The energy stored in the inductance is  $U_L = \frac{1}{2}L(|I|\cos \omega t)^2$ .

The energy stored in the capacitor is  $U_c = \frac{1}{2}C\left[|V_c|\cos\left(\omega t - \frac{\pi}{2}\right)\right]^2 = \frac{1}{2}\frac{1}{\omega^2 C}(|I|\sin \omega t)^2$ .

At resonance,  $\omega_0 = \frac{1}{\sqrt{LC}}$ , we have

$$U_L + U_c = \frac{1}{2}L(|I|\cos \omega t)^2 + \frac{1}{2}\frac{1}{\omega^2 C}(|I|\sin \omega t)^2 = \frac{1}{2}L|I|^2.$$

The energy dissipated by the resistor per cycle is

$$U_R = \int_0^T (|I| \cos \omega_0 t)^2 R dt = \frac{1}{2} |I|^2 R T = \frac{1}{2} |I|^2 R \times \frac{2\pi}{\omega_0}.$$

After these preparations, the Q factor is now

$$\begin{aligned} Q &= \frac{2\pi \times \text{stored energy}}{\text{dissipated energy per cycle}} = \frac{2\pi \times (U_L + U_C)}{U_R} \\ &= \frac{2\pi \times \frac{1}{2} L |I|^2}{\frac{1}{2} |I|^2 R \times \frac{2\pi}{\omega_0}} = \frac{\omega_0 L}{R} = \frac{1}{\omega_0 C R} = \frac{|X_L|}{R} = \frac{|X_C|}{R} = \frac{1}{R} \sqrt{\frac{L}{C}}. \end{aligned}$$

The bandwidth is given by  $\Delta\omega = \omega_2 - \omega_1$ , where  $\omega_1$  and  $\omega_2$  satisfy  $\frac{|I(\omega_{1,2})|^2}{|I|_{\max}^2} = \frac{1}{2}$ .

$$\text{From } |I| = \frac{|V_s|/R}{\sqrt{1 + \left(\omega L - \frac{1}{\omega C}\right)^2 / R^2}} \text{ above, this means } \omega L - \frac{1}{\omega C} = \pm R.$$

$$\text{The solution is easily found to be } \omega_{2,1} = \frac{\pm RC + \sqrt{(RC)^2 + 4LC}}{2LC}.$$

Therefore,  $\Delta\omega = \omega_2 - \omega_1 = \frac{R}{L}$ . When measured by frequency, we have the bandwidth

$$\Delta f = \frac{1}{2\pi} \frac{R}{L} = \frac{f_0}{Q}, \text{ and the famous relation of } Q = \frac{f_0}{\Delta f}.$$

Pengqian Wang

September 22, 2025